

CSEE 4270 Report: Final Project

Victor Philippe

School of Electrical and Computer Engineering

University of Georgia

Vlp47226@uga.edu

Contributions: Please list contributions (in estimated percentages) of each member in the following categories.

- Pre-lab design and analysis: Philippe
- In-lab module and testbench design: Philippe
- In-lab testbench simulation and analysis: Philippe
- In-lab FPGA synthesis and analysis: Philippe
- Lab report writing: Philippe

Abstract

The final project provides a new extension of state machines with a look at High Level State Machine (HLSM) to simulate a visual reaction timer. Here, multiple components including a clock divider and a pseudo random number generator are designed and simulated using a testbench in Verilog in the Xilinx environment. This lab introduces new concepts like pseudo random number generation as well as another state machine using HLSM through its design and simulation.


1. INTRODUCTION

The reaction timer will measure a user's reaction time by counting the time elapsing after the user has reacted and pushed a button after a pseudo random amount of time has elapsed. The reaction has two smaller components that are the clock divider to slow the speed of the device down as well as a module dedicated to generating random numbers. The HLSM will be implemented using one-procedure and feature a behavioral approach as well. The sequence of events that governs this particular HLSM can be seen in Figure 1. Similarly, the high level diagram of the project is shown in Figure 2.

Figure 1: Sequence of events of HLSM

- List of events for ReactionTimer
1. Start the program/device
 2. go to initial/waiting msg state
wait for display
 3. Wait for random value time
 4. If pressed too fast,
go to cheer msg
 5. If pressed too slow
go to slow msg
 6. end the wait
 7. go to step 1

Figure 2: Diagram of HLSM

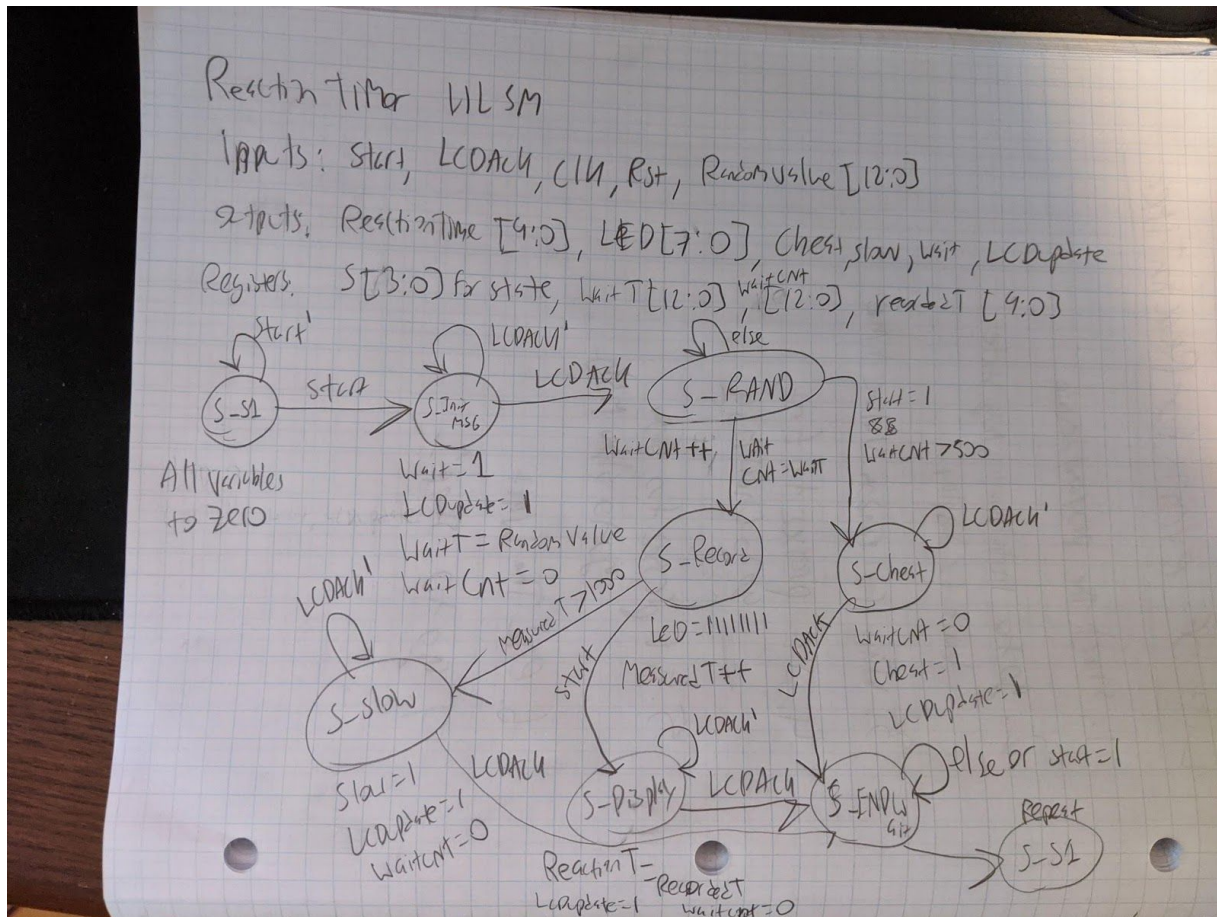

2. IMPLEMENTATION

The first lower level module to be designed and implemented was the clock divider. This clock divider was tasked with taking in a 50 MHz clock signal and converting it to 1KHz. It's behavioral design is shown in figure 3. Figure 4 demonstrates the test bench for the clock cycles as it shows a complete cycle in 1ms. Figure 5 and 6 show the behavioral design and testbench for the pseudo random number generator. Figure 7 and 8 show the design of the HLSM as well its testbench without the number generator and with it. The simulations of these test benches will be shown in the Experimental Results section.

Figure 3: Verilog module for clock divider

```
module ClkDiv(Clk, DivReset, ClkOut);
    input Clk, DivReset;
    output reg ClkOut;
    reg ClkInt;
    reg[24:0] Count;
    parameter Value = 24999;
```

```
always @(posedge Clk) begin
    if( DivReset == 1 )begin
        Count <= 0;
        ClkOut <= 0;
        ClkInt <= 0;
```



```
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
    @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
    @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
    @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
    @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
```



```

//local variables
reg [12:0] Val;
reg [12:0] Counter = 0;

always @(posedge Clk) begin
    if (Rst == 1) begin
        Val = MinValue;
    end
    else begin
        if (Counter % 2 == 0) begin //if Counter is even
            Counter = 2* Counter + 3;
        end else begin //if Counter is odd
            Counter = 3 * Counter + 4;
        end
        Val = Val + Counter; //makes a psuedo random number
        if (Val > MaxValue) begin //if the number too big
            Val = MinValue;
        end
        if (Val < MinValue) begin //if the bumber too small
            Val = MaxValue;
        end
    end
end
end
assign RandomValue = Val;
endmodule

```

Figure 6: Testbench for PRNG

```

module RandomGen_tb();

    reg Clk_s, Rst_s;
    wire [12:0] RandomValue_s;

    RandomGen RandomGen_1(Clk_s, Rst_s, RandomValue_s);

    always begin
        Clk_s <= 0;
        #10;
        Clk_s <= 1;
        #10;
    end
end

```

[illegible]


```
        @(posedge Clk_s);
        @(posedge Clk_s);
    @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
    @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
    @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
    @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
    @(posedge Clk_s);
        @(posedge Clk_s);
```

```

        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
        @(posedge Clk_s);
    end

endmodule

```

Figure 7: HSLM Verilog module

```

module ReactionTimer(Clk, Rst, Start, LED, ReactionTime, Cheat, Slow, Wait, RandomValue,
LCDUpdate, LCDAck);

```

```

    //variables
    input Start, LCDAck, Clk, Rst;
    input [12:0] RandomValue;
    output reg [9:0] ReactionTime;
    output reg [7:0] LED;
    output reg Cheat, Slow, Wait;
    output reg LCDUpdate;
    //local variables
    reg [3:0] S;
    reg [12:0] WaitT;
    reg [12:0] WaitCnt;
    reg [9:0] RecordedT;
    //constants
    parameter S_S1 = 0, S_InitMsg = 1, S_Rand = 2, S_Record = 3, S_Cheat = 4, S_Slow = 5,
        S_Display = 6, S_EndWait = 7;

    always @(posedge Clk) begin
        if (Rst == 1) begin
            S <= S_S1;

            Cheat <= 0;
            Slow <= 0;
            Wait <= 0;
            LED <= 0;
            WaitT <= 0;

```

```

        WaitCnt <= 0;
        RecordedT <= 0;
        ReactionTime <= 0;
        LCDUpdate <= 0;
    end
else begin
    // Default Values
    Cheat <= 0;
    Slow <= 0;
    LED <= 0;
    Wait <= 0;
    ReactionTime <= 0;
    LCDUpdate <= 0;

    case (S)
        S_S1: begin
            RecordedT <= 0;
            if (Start == 1) begin
                S <= S_InitMsg;
            end
            else begin
                S <= S_S1;
            end
        end

        S_InitMsg: begin
            Wait <= 1;
            LCDUpdate <= 1;
            if (LCDAck == 1) begin
                WaitT <= RandomValue;
                WaitCnt <= 0;
                S <= S_Rand;
            end
            else begin
                S <= S_InitMsg;
            end
        end

        S_Rand: begin

```

```

        if (Start == 1 && WaitCnt > 500 ) begin
            S <= S_Cheat;
        end
        else if( WaitCnt == WaitT ) begin
            LED <= 8'hFF;
            S <= S_Record;
        end
        else begin
            WaitCnt <= WaitCnt + 1;
            S <= S_Rand;
        end
    end
end

```

```

S_Record: begin
    LED <= 8'hFF;
    if (Start == 1) begin
        S <= S_Display;
    end
    else if( RecordedT >= 1000 ) begin
        S <= S_Slow;
    end
    else begin
        RecordedT <= RecordedT + 1;
        S <= S_Record;
    end
end
end

```

```

S_Cheat: begin
    Cheat <= 1;
    LCDUpdate <= 1;
    if (LCDAck == 1) begin
        WaitCnt <= 0;
        S <= S_EndWait;
    end
    else begin
        S <= S_Cheat;
    end
end
end

```

```

S_Slow: begin
    Slow <= 1;
    LCDUpdate <= 1;
    if (LCDAck == 1) begin
        WaitCnt <= 0;
        S <= S_EndWait;
    end
    else begin
        S <= S_Slow;
    end
end

S_Display: begin
    ReactionTime <= RecordedT;
    LCDUpdate <= 1;
    if (LCDAck == 1) begin
        WaitCnt <= 0;
        S <= S_EndWait;
    end
    else begin
        S <= S_Display;
    end
end

S_EndWait: begin
    if (Start == 1) begin
        S <= S_EndWait;
    end
    else if( WaitCnt == 1000 ) begin
        S <= S_S1;
    end
    else begin
        WaitCnt <= WaitCnt + 1;
        S <= S_EndWait;
    end
end

default: begin
    S <= S_S1;

```

```

                                WaitT <= 0;
                                RecordedT <= 0;
                                end
                                endcase
                                end
                                end
                                endmodule

```

Figure 8: a) testbench without RandomGen

```

module ReactionTimer_tb();
    reg Clk_s, Rst_s, Start_s, LCDAck_s;
    reg [12:0] RandomValue_s;
    wire LCDUpdate_s, Cheat_s, Slow_s, Wait_s;
    wire [9:0] ReactionTime_s;
    wire [7:0] LED_s;

    ReactionTimer ReactionTimer_1(Clk_s, Rst_s, Start_s, LED_s, ReactionTime_s, Cheat_s,
    Slow_s, Wait_s, RandomValue_s, LCDUpdate_s, LCDAck_s);

    always begin
        Clk_s <= 0;
        #10;
        Clk_s <= 1;
        #10;
    end

    initial begin
        RandomValue_s <= 700;
        #5 Rst_s <= 1; Start_s <= 1; LCDAck_s <= 1;
        @(posedge Clk_s);
        #5 Rst_s <= 0;
        @(posedge Clk_s);
        #40 LCDAck_s <= 0;
        @(posedge Clk_s);
        #10135 LCDAck_s <= 1; Start_s <= 0;
        @(posedge Clk_s);
        #10000 RandomValue_s <= 300;
        @(posedge Clk_s);
        #24815 Start_s <= 1;
        @(posedge Clk_s);
    end

```

```

        #6500 Start_s <= 0;
        #5 LCDAck_s <= 0;
        @(posedge Clk_s);
        #20495 Start_s <= 1; LCDAck_s <= 1;
        @(posedge Clk_s);
        #100 Start_s <= 0; LCDAck_s <= 0;
        @(posedge Clk_s);
        #26100 LCDAck_s <= 1;
        @(posedge Clk_s);
    end
endmodule

```

endmodule

b) testbench with randomGen

```

module RandomTimerWGen_tb();

reg Clk_s, Rst_s, Start_s, LCDAck_s;
    wire [12:0] RandomValue_s;
    wire LCDUpdate_s, Cheat_s, Slow_s, Wait_s;
    wire [9:0] ReactionTime_s;
    wire [7:0] LED_s;
    RandomGen RandomGen_1(Clk_s, Rst_s, RandomValue_s);
    ReactionTimer ReactionTimer_1(Clk_s, Rst_s, Start_s, LED_s, ReactionTime_s, Cheat_s,
    Slow_s, Wait_s, RandomValue_s, LCDUpdate_s, LCDAck_s);

    always begin
        Clk_s <= 0;
        #10;
        Clk_s <= 1;
        #10;
    end

    initial begin
        #5 Rst_s <= 1; Start_s <= 1; LCDAck_s <= 1;
        @(posedge Clk_s);
        #5 Rst_s <= 0;
        @(posedge Clk_s);
        #40 LCDAck_s <= 0;
        @(posedge Clk_s);
    end
endmodule

```

```

#20 Start_s <= 0;
@(posedge Clk_s);
#20 LCDAck_s <= 1;
@(posedge Clk_s);
#20 Start_s <= 1;
@(posedge Clk_s);
#20 LCDAck_s <= 0;
@(posedge Clk_s);
#20 Start_s <= 1;
@(posedge Clk_s);
#20 LCDAck_s <= 1;
@(posedge Clk_s);
#20 Start_s <= 1;
@(posedge Clk_s);
#10000 LCDAck_s <= 1; Start_s <= 0;
@(posedge Clk_s);
#20020 Start_s <= 1;
#40 Start_s <= 0;
@(posedge Clk_s);
#40000 LCDAck_s <= 0; Start_s <= 1;
@(posedge Clk_s);
#5000 LCDAck_s <= 1; Start_s <= 0;
@(posedge Clk_s);
#24815 Start_s <= 0;
@(posedge Clk_s);
#6500 Start_s <= 0;
#5 LCDAck_s <= 0;
@(posedge Clk_s);
#40 Start_s <= 0;
@(posedge Clk_s);
#60 Start_s <= 1;
@(posedge Clk_s);
#20495 Start_s <= 0; LCDAck_s <= 1;
@(posedge Clk_s);
#100 Start_s <= 0; LCDAck_s <= 0;
@(posedge Clk_s);
#25000 LCDAck_s <= 1; Start_s <= 0;
@(posedge Clk_s);

```

end

endmodule

3. EXPERIMENTAL RESULTS

The first tested component was the clock divider which needed to show a complete cycle of 1ms over the waveform. Figure 9 shows that from the start of the simulation the clock out does not go high until around 0.5ms (500us) and then goes to 0 shortly after 1ms(1000us). This shows a complete cycle of low then high then low for the waveform, proving its competence. Figure 10 moves onto the next module to test which is the random number generator. The test bench needed to show that random or effectively random numbers were generated. This is the case as my alternating equations and separate counter resulted in this phenomena. Figure 11 goes into the reaction timer elements and starts with the waveform without the random gen. Here, the waveform starts with a complete reset of the system. Then, it starts the first test which is to provide a cheating response. This is done with a random value of greater than 500 and start being high. Once it goes through the cheating sequence and through the end wait, it starts the next test. This is to correctly measure the reaction time. After it comes back to the start, it does the last test of measuring a slow reaction

Figure 9: Waveform for clock divider

 


Figure 10: Waveform for PRNG



 



Figure 11: Waveform for ReactionTimer without random Gen

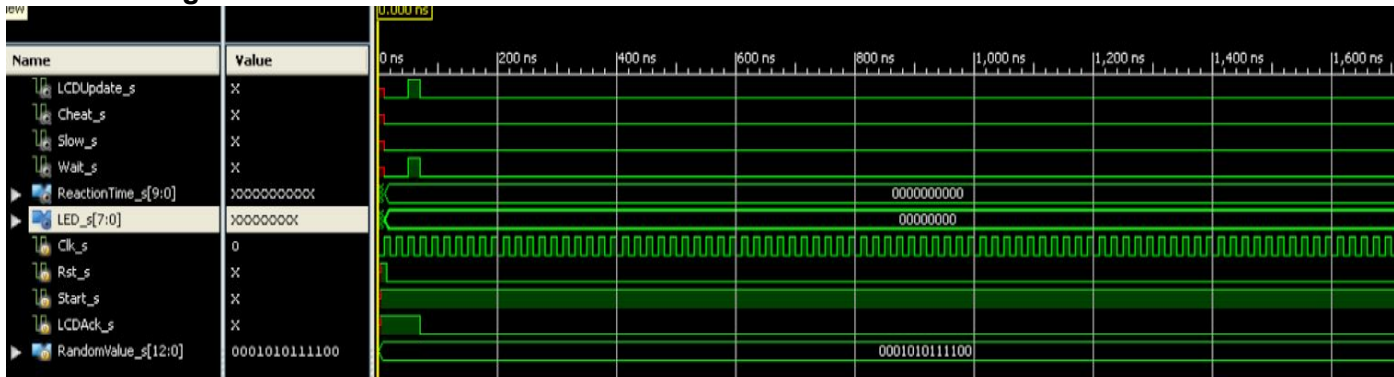

 
The first reset is done and the first steps toward calculating the WaitCnt is done toward the cheat section



 
Cheat has been accomplished and now we are in the end wait state and will do another measurement
 The randomValue value is then changed a short while later to do a measurement that will not be caught by another state



 
We reached the waiting state and are now in the random state



 
The LED lights up to indicate that the waitcnt reached the time needed to wait and LCDUpdate goes high to indicate that the time has been recorded.



 The testbench made it back to the waiting state after recording and finishing. Now it is on to testing the slow function




 The LED has become lit to indicate we are in the measuring state



The LED turns off and the slow state is enacted and LCDAck is set back to high to go to the end wait and initial state eventually finishing the testing

B) ReactionTimer with RandomGen

 

First we start by getting to our wait state and starting our first test for cheat



We get to cheat state so we exit through the end state and come back to wait eventually



This is the wait state where we will now attempt to record the reaction time



We successfully got to the LED turning on state




Reaction timer is set now and we update the LCD



We now end that state to test our last state of being too slow



 We get back to the wait state to prepare for slow



We are now measuring the reaction time



We were too slow so it displayed the slow state

